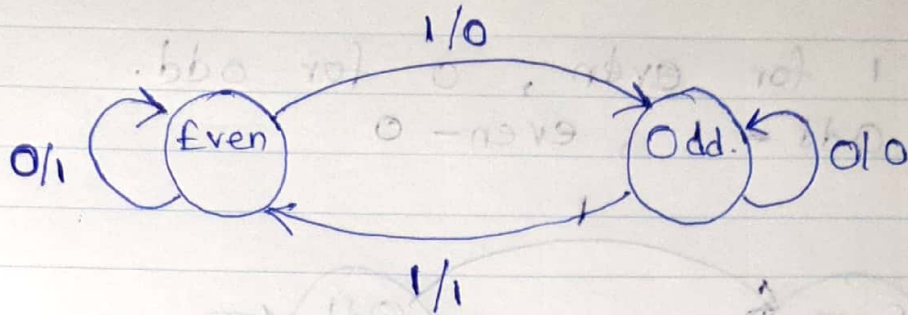


## ① Mealy model.



Output : is 1 for even, 0 for Odd.

States : Odd - 1, Even - 0


State Table

Present State	Input	Next State	Present Output
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

D flip flops are used. (Flip Flop input = Next state).

$$\text{Flip Flop input} = (\text{Present State}) \text{ XOR } (\text{Input})$$

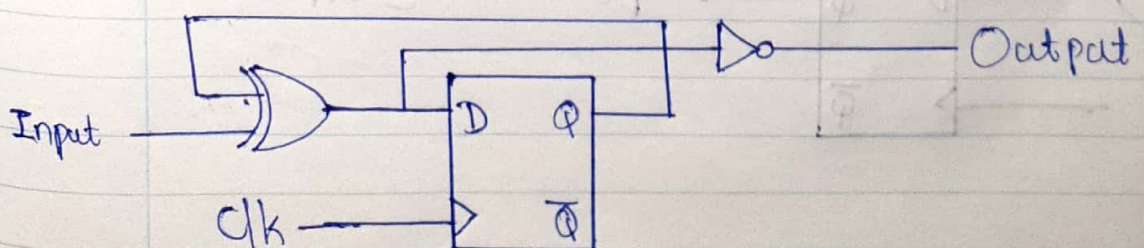
$$\text{Flip Flop Output} = \left[ (\text{Present State}) \text{ XOR } (\text{Input}) \right]'$$



# Moore Model.

Output: 1 for even, 0 for odd.

States: Odd - 1, even - 0

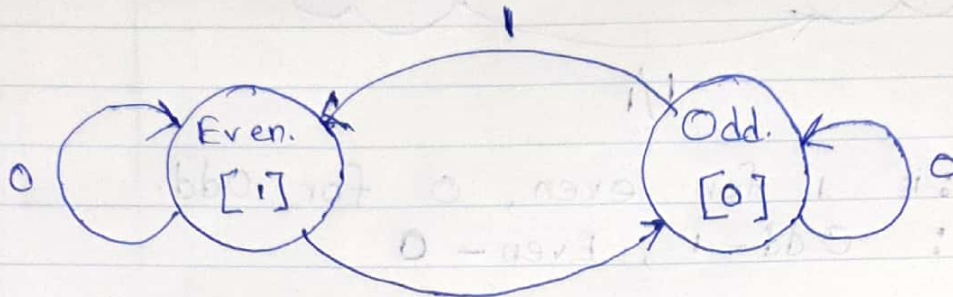


Present State	Input	Next State	Present Output
0	0	0	1
0	1	1	1
1	0	1	0
1	1	0	0

1 flip fops are used. (Flip Flop input = Next State.)

$$\text{Flip Flop input} = (\text{Present state}) \text{ XOR } (\text{Input})$$
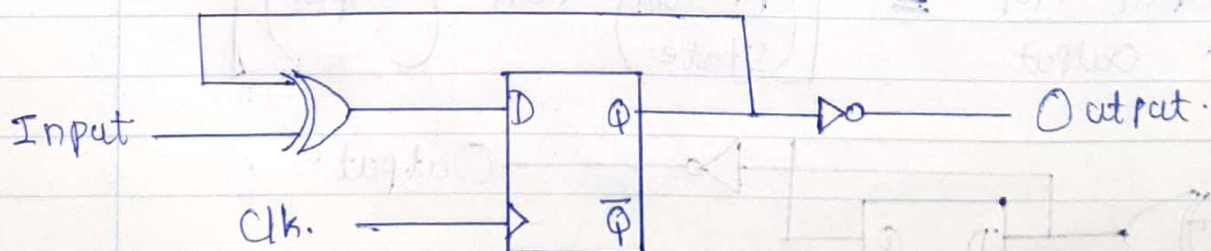
$$\text{Flip Flop output} = (\text{Present State})'$$





- ②. Output  $z = 1$  if '011' detected.  
 Output  $z = 0$  if otherwise.


A is considered as the initial state.,  $z = 0$ .

A : —

B : 0\_ ,  $z = 0$ .

C : 01\_ ,  $z = 0$ .

D : 011 ,  $z = 1$

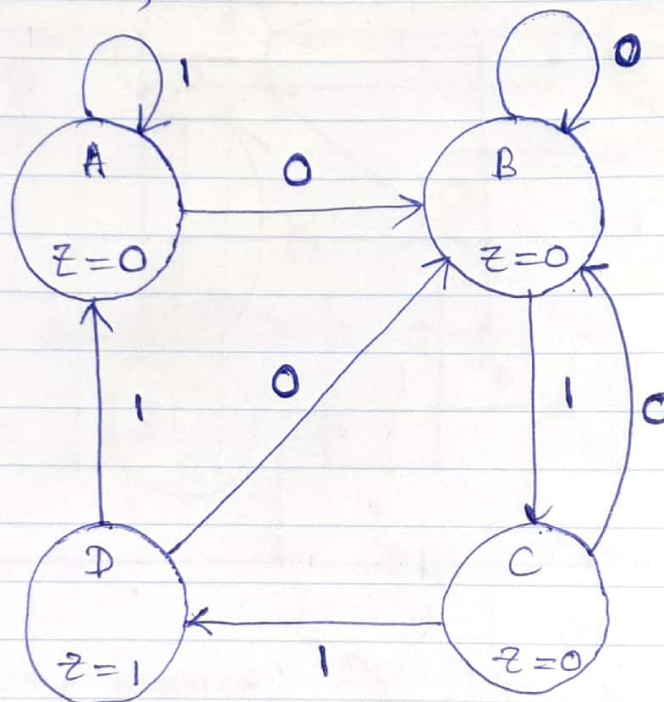

State Table.

consider,

$$A = 00$$

$$B = 01$$

$$C = 10$$

$$D = 11$$

Characteristic Equation of a D flip flop,

$$D = Q(t + \epsilon)$$

Atisa

State Table.

Present State.			Input $I$	Next State.		Output $Z$	Flip Flop Inputs.	
	$Q_1(t)$	$Q_2(t)$		$Q_1(t+1)$	$Q_2(t+1)$		$D_1 = Q_1(t+1)$	$D_2 = Q_2(t+1)$
A	0	0	0	B	0	1	0	1
A	0	0	1	A	0	0	0	0
B	0	1	0	B	0	1	0	1
B	0	1	1	C	1	0	1	0
C	1	0	0	B	0	1	0	1
C	1	0	1	D	1	1	1	1
D	1	1	0	B	0	1	0	1
D	1	1	1	A	0	1	0	0

K map for  $D_1$ .

$Q_1 \backslash Q_2 I$				
	00	01	11	10
0	0	0	1	0
1	0	1	0	0

$$D_1 = Q_1' Q_2 I + Q_1 Q_2' I$$

$$D_1 = I (Q_1' Q_2 + Q_1 Q_2')$$

$$D_1 = I (Q_1 \oplus Q_2)$$

K map for  $D_2$ 

$Q_1 \backslash Q_2 I$				
	00	01	11	10
0	1	0	0	1
1	1	1	0	1

$$D_2 = I' + Q_1 Q_2'$$

$$Z = Q_1 \cdot Q_2$$







- ③ Since ~~they~~ there are 3 bits, 3 D flip flops has to be used.

Characteristic :  $Q(t+1) = D$

Equation

(D flip flops).

Present State.			Next State.			Flip Flop Inputs.		
$Q_C(t)$	$Q_B(t)$	$Q_A(t)$	$Q_C(t+1)$	$Q_B(t+1)$	$Q_A(t+1)$	$D_C$	$D_B$	$D_A$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	0
1	0	0	1	0	1	1	0	1
1	0	1	1	1	0	1	1	0
1	1	0	1	1	1	1	1	1
1	1	1	0	0	0	0	0	0

K Map for the  $D_C$ .

$Q_C \backslash Q_B Q_A$	00	01	11	10
0	0	0	1	0
1	1	1	0	1

$$D_C = Q_B' Q_C + Q_A' Q_C + Q_C' Q_A Q_B$$

$$D_C = Q_C (Q_A' + Q_B') + Q_C' (Q_A \cdot Q_B)$$

$$D_C = Q_C (Q_A \cdot Q_B)' + Q_C' (Q_A \cdot Q_B)$$

$$D_C = Q_C \oplus (Q_A \cdot Q_B) //$$

K Map for the  $D_B$

$Q_C \backslash Q_B Q_A$	00	01	11	10
0	0	1	0	1
1	0	1	0	1


$$D_B = Q_B' Q_A + Q_B Q_A'$$

$$D_B = Q_A \oplus Q_B //$$



240 K Map for  $D_A$ .

$Q_C$ \ $Q_B Q_A$	00	01	11	10
0	1	0	0	1
1	1	0	0	1

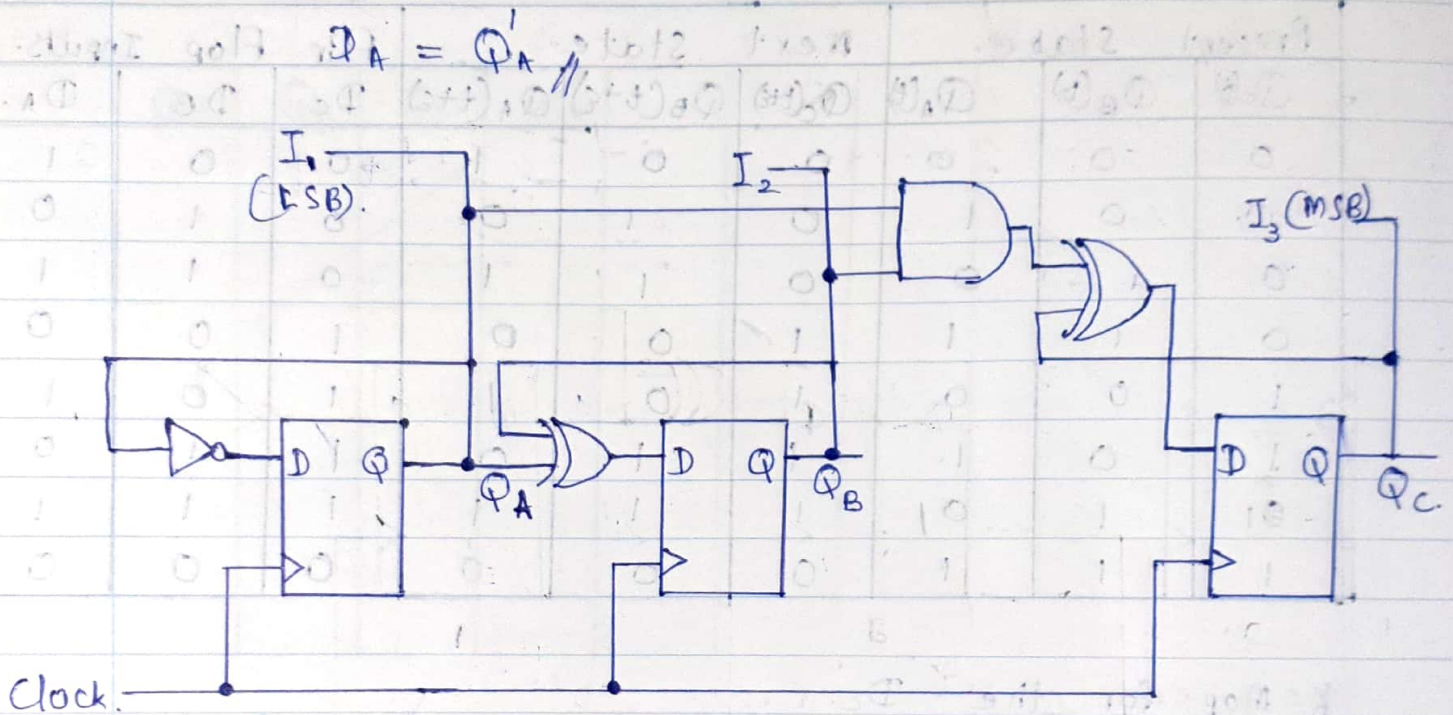

Positive edge triggered flip flops are used here.

$Q_A$	$Q_B$	$Q_C$	$I_1$	$I_2$	$I_3$
0	0	0	0	0	0
1	0	0	1	0	0
0	1	0	0	1	0
1	1	0	1	1	0
0	0	1	0	0	1
1	0	1	1	0	1
0	1	1	0	1	1
1	1	1	1	1	1